

1.

a.  $\Delta V = 9 - (3)(1) = 6V$

b.  $12 = \frac{6^2}{R_2} \quad R_2 = 3 \Omega$

c.  $R_1 \text{ AND } R_2 = \frac{6}{3} = 2 \Omega$

$$\frac{1}{R_1} + \frac{1}{3} = \frac{1}{2} \quad R_1 = 6 \Omega$$

2.

$$a. \quad \frac{1}{4} + \frac{1}{4} + \frac{1}{2} = \frac{1}{R_{EQ}}$$

$$R_{EQ} = 1 \Omega$$

$$\Sigma R = 8 \Omega$$

$$I_{CIRCUIT} = \frac{48}{8} = 6 A$$

$$\Delta V_{PARALLEL} = -6 V$$

RESISTORS

$$I_{2\Omega} = 3 A$$

$$b. \quad P = -I^2 \cdot R = -(6^2)(3) = -108 W$$

$$c. \quad \Delta V = \mathcal{E} - I \cdot r$$

$$= -12 - (6)(1) = -18 V$$

BOTH NEGATIVE IF  
CURRENT FLOWS  
LEFT TO RIGHT

3.

$$a. \quad \frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{6} \quad R_{eq} = 4 \Omega$$

$$-18 = -(2)(R+4)$$

$$R = 5 \Omega$$

$$b. \quad \Delta V_{\text{PARALLEL RESISTORS}} = -(2)(4) = -8V$$

$$i. \quad I = 8/6 = 4/3 A$$

$$ii. \quad I = 8/12 = 2/3 A$$

$$c. \quad V_B = +10V \quad V_C = -10V \quad V_D = -2V$$

$$d. \quad P = I \cdot \Delta V = (2)(20) = 40 W$$

4.

a.  $\frac{1}{4} + \frac{1}{12} = \frac{1}{R} \quad R = 3 \Omega$

$$\Sigma R = 3 + 9 = 12 \Omega$$

b.  $V = (I)(R) = (0.4)(12) = 4.8 \text{ V}$

c.  $\Delta V_{R3} = -(0.4)(9) = -3.6 \text{ V}$  so  $\Delta V_{R1} = -1.2 \text{ V}$

d.  $P = \frac{-\Delta V^2}{R} = \frac{-1.2^2}{4} = -0.36 \text{ W}$

e.  $Q = I \cdot \Delta t = (0.4)(60) = 24 \text{ C}$

5.

$$a. \quad \frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{4+8}$$

$$R_{eq} = 6 \Omega$$

$$b. \quad I = \frac{24V}{12 \Omega} = 2A$$

$$c. \quad \Delta V_T = \mathcal{E} - I \cdot r = 24 - (2)(1) = 22V$$

$$d. \quad \frac{\Delta E}{\Delta t} = P = -I^2 R = -(2^2)(12) = -12W$$

$$e. \quad \Delta V = -I \cdot R = -(2)(6) = -12V$$

$$f. \quad P = I \cdot \Delta V = (2A)(22V) = 44W$$

6.


a.  $\mathcal{E}$  IS  $\Delta V$  WHEN  $I = 0$ , SO THIS IS THE Y-INTERCEPT OF THE GRAPH, 4.5 V.

b.  $\Delta V = \mathcal{E} - I \cdot r$ , SO  $r$  IS THE NEGATIVE OF THE GRAPH'S SLOPE.  $r = 0.5 \Omega$ .


c.  $\frac{4.5}{3} = R + 0.5$  SO  $R = 1 \Omega$

d. IF  $R_{\text{EXT}} = 0$ ,  $I = \frac{4.5}{0.5} = 9 \text{ A}$


e.

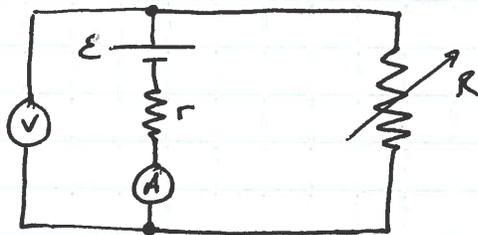

7. a.

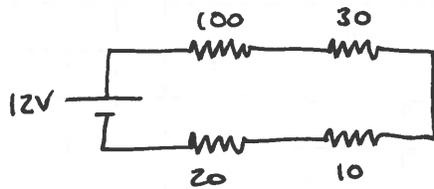

b.

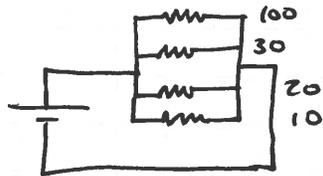

c. i.  $\frac{1}{R_{eq}} = \frac{1}{100} + \frac{1}{20+30}$   $R_{eq} = 33.\bar{3} \Omega$

$$\Sigma R = 43.\bar{3} \Omega$$

$$I = \frac{12}{43.3} = 0.277 A$$

ii.  $P = I \cdot \Delta V = (0.277)(12) = 3.323 W$

d.  $\Delta t = \frac{E}{P} = \frac{10,000}{3.323} = 3009 s$

8.

$$a. \quad \frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3} \quad R_{eq} = 2 \Omega$$

$$\Sigma R = 5 \Omega \quad I = \frac{9}{5} = 1.8 A$$

$$b. \quad P_A = -1.8^2 \cdot 3 = -9.72 W$$

$$V_A = -5.4 V \text{ so } V_B = V_C = -3.6 V$$

$$P_B = -\frac{3.6^2}{6} = -2.16 W \quad P_C = \frac{-3.6^2}{3} = -4.32 W$$

BULB A IS BRIGHTEST.

c. BULB C DROPS TO ZERO BRIGHTNESS, AS THE CURRENT THROUGH IT DROPS TO ZERO.

BULB A DROPS IN BRIGHTNESS BECAUSE THE TOTAL RESISTANCE OF THE CIRCUIT INCREASES, DECREASING THE CURRENT THROUGH A.

BULB B INCREASES IN BRIGHTNESS. CURRENT THROUGH A DECREASES, SO  $\Delta V_A$  ALSO DECREASES.  $\Delta V_B$  MUST THEN INCREASE, SO ITS POWER DOES ALSO.

9.

- a.
- 1  $I_A$
  - 2  $I_C$
  - 3  $I_B$

$$I_A = I_C + I_B \text{ so } I_A \text{ IS GREATEST}$$

$$\Delta V_B = \Delta V_C \text{ AND } R_C \text{ IS LESS THAN } R_B$$

$$\text{so } I_C > I_B$$

- b.
- 1 A
  - 2 B
  - 3 C
- } EQUAL

$$\Delta V = -I \cdot R \text{ AND A HAS THE HIGHEST CURRENT AND RESISTANCE}$$

$$\Delta V_B = \Delta V_C \text{ BECAUSE THEY ARE IN-PARALLEL}$$

c.

$$\frac{1}{R_{eq}} = \frac{1}{400} + \frac{1}{200} \quad R_{eq} = 133.\bar{3} \Omega$$

$$\Sigma R = 133.\bar{3} + 400 = 533.\bar{3} \Omega$$

d.

$$I_{loop} = \frac{12}{533.\bar{3}} = 0.0225 \text{ A}$$

$$\Delta V_A = -(0.0225)(400) = -9 \text{ V}$$

$$\text{so } \Delta V_C = -3 \text{ V}$$

$$I_C = \frac{3}{200} = 0.015 \text{ A}$$